

5.6 章末問題解答

5.1

(1)

$$\begin{aligned}|1 - j3| &= \sqrt{10}, \\ 1 - j3 &= \sqrt{10}(\cos 71.6^\circ - j \sin 71.6^\circ)\end{aligned}$$

(2)

$$\begin{aligned}\left| \frac{1+j}{1-j} \right| &= 1, \\ \frac{1+j}{1-j} &= 1(\cos 90^\circ + j \sin 90^\circ)\end{aligned}$$

(3)

$$\begin{aligned}\left| \frac{c+jd}{a+jb} \right| &= \sqrt{\frac{c^2+d^2}{a^2+b^2}}, \\ \frac{c+jd}{a+jb} &= \sqrt{\frac{c^2+d^2}{a^2+b^2}} \left\{ \cos \left(\tan^{-1} \frac{ad-bc}{ac+bd} \right) + j \sin \left(\tan^{-1} \frac{ad-bc}{ac+bd} \right) \right\}\end{aligned}$$

5.2

$$\theta = 54.2^\circ$$

ベクトル図は省略

5.3

(1)

$$10 \angle 60^\circ = 5 + j5\sqrt{3}$$

(2)

$$16 \angle 210^\circ = -8\sqrt{3} - j8$$

5.4

(1)

$$\dot{z}_1 \cdot \dot{z}_2 = j600$$

(2)

$$\dot{z}_1^3 = -1000$$

(3)

$$\frac{\dot{z}_1}{\dot{z}_2} = \frac{\sqrt{3}}{12} + j \frac{1}{12}$$

5.5

(省略)

5.6

(a)

$$\dot{I}_1 = 10\angle 53.1^\circ, \quad I_1 = 10 \text{ [A]}$$

$$\dot{I}_2 = 5, \quad I_2 = 5 \text{ [A]}$$

$$\dot{I} = 11 + j8 = 13.6\angle 36.0^\circ, \quad I = 13.6 \text{ [A]}$$

(b)

$$P = 550 \text{ [W]}$$

5.7

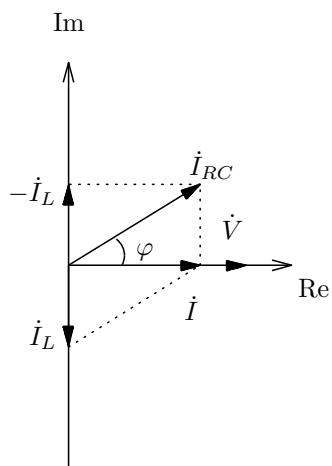


図1 問題 5.7(a) のベクトル図

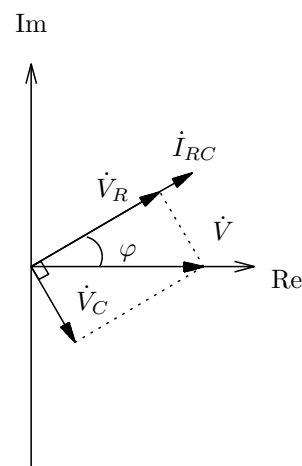


図2 問題 5.7(b) のベクトル図

5.8

$$R = 17.3 \text{ } [\Omega], \quad C = 318 \text{ } [\mu F]$$

5.9

(a)

$$\dot{Y} = 0.053\epsilon^{j30^\circ}$$

(b) 抵抗とキャパシタの並列回路であり,

$$R = 21.8 \text{ } [\Omega], \quad C = 70.3 \text{ } [\mu F]$$

5.10

$$\dot{Z} = 5 + j9.32, |\dot{Z}| = 10.6$$

5.11

(a)

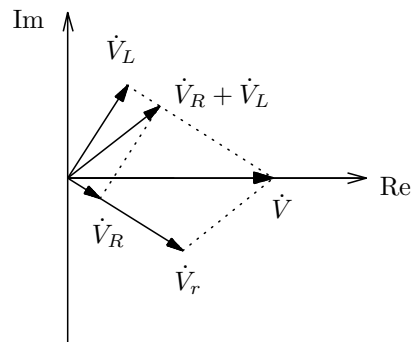


図3 問題 5.11 のベクトル図

(b)

$$R = 4.93 [\Omega], X_L = 10.1 [\Omega]$$

5.12

(a)

$$\dot{I} = 20 \angle 36.86^\circ$$

(b)

$$\begin{aligned}\dot{V}_1 &= 80 \angle 36.86^\circ \\ \dot{V}_2 &= 60 \angle 126.96^\circ \\ \dot{V}_3 &= 120 \angle -53.1^\circ\end{aligned}$$

5.13

(a)

$$\begin{aligned}\dot{I}_1 &= 5 \\ \dot{I}_2 &= 10 \angle -53.13^\circ \\ \dot{I}_3 &= 5 \angle 36.86^\circ \\ \dot{I} &= \dot{I}_1 + \dot{I}_2 + \dot{I}_3 = 15.8 \angle -18.4^\circ\end{aligned}$$

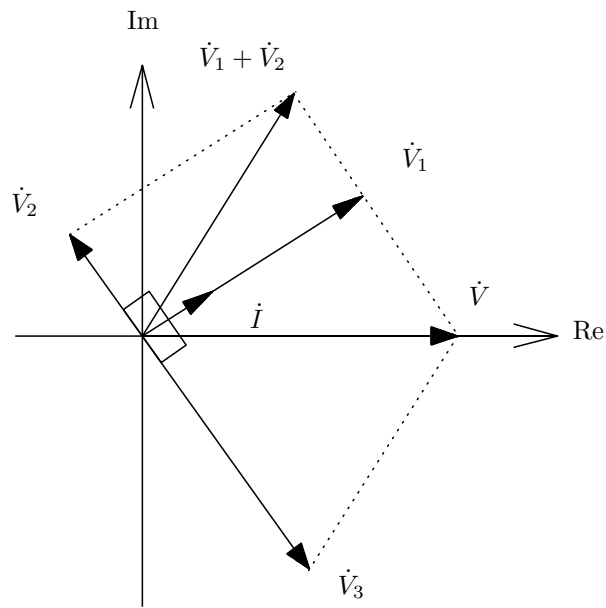


図4 問題 5.12 のベクトル図

(b)

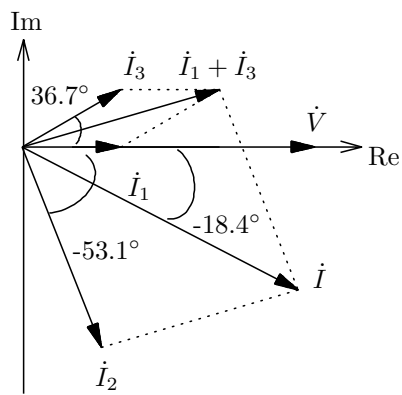


図5 問題 5.13 のベクトル図

5.14

$$\dot{Z} = 5 + j9.3$$

5.15

$$|\dot{I}| = 20.6 \text{ [A]}$$

5.16

$$P = \frac{1}{T} \int_0^T \sqrt{2}V \sin \omega t \cdot \sqrt{2}I \sin(\omega t + \varphi) dt = VI \cos \varphi$$

5.17

$$I = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \sqrt{\frac{I_m^2}{T} \int_0^T \sin^2(\omega t + \varphi) dt} = \sqrt{\frac{I_m^2}{2}}, \rightarrow I_m = \sqrt{2}I$$

5.18

(a)

$$P = \frac{R}{R^2 + \left(\frac{1}{\omega C}\right)^2} V^2$$

(b)

$$P = \frac{V^2}{R}$$

5.19

(a)

$$\begin{aligned} \dot{I}_L &= \frac{\dot{V}}{r + j\omega L}, \quad \dot{I}_C = j\omega C \dot{V} \\ \dot{I} &= \dot{I}_L + \dot{I}_C = \left(\frac{1}{r + j\omega L} + j\omega C \right) \dot{V} \end{aligned}$$

(b)

$$\cos \varphi = \frac{r}{\sqrt{r^2 + \omega^2 \{L(1 - \omega^2 LC) - r^2 C\}^2}}$$

(c)

$$r = \sqrt{\frac{L(1 - \omega^2 LC)}{C}}$$

5.20

$$R_L = \sqrt{r^2 + (\omega L)^2}$$

5.21

$$R_L = 10.0 \text{ } [\Omega], \quad |\dot{I}_R| = 5.0 \text{ } [\text{A}], \quad P = 250.0 \text{ } [\text{W}]$$

5.22

$$f = 116.0 \text{ [Hz]}$$

5.23

$$R = 20.0 \text{ } [\Omega]$$

5.24

$$\omega = \frac{1}{\sqrt{LC}}$$

5.25

(a)

$$\dot{I} = \frac{\dot{V}}{(r + jx)(1 - \omega^2 CL) + j\omega L} = \frac{\dot{V}}{r(1 - \omega^2 LC) + j\{x(1 - \omega^2 LC) + \omega L\}}$$

(b)

$$\omega = \frac{1}{\sqrt{LC}}, \quad |\dot{I}| = \frac{|\dot{V}|}{\omega L} = \sqrt{\frac{C}{L}} |\dot{V}|$$